




# ANSWER SHEET

## Problem E1



ii. (0.7 pts) Graph:  $y$  versus  $x$

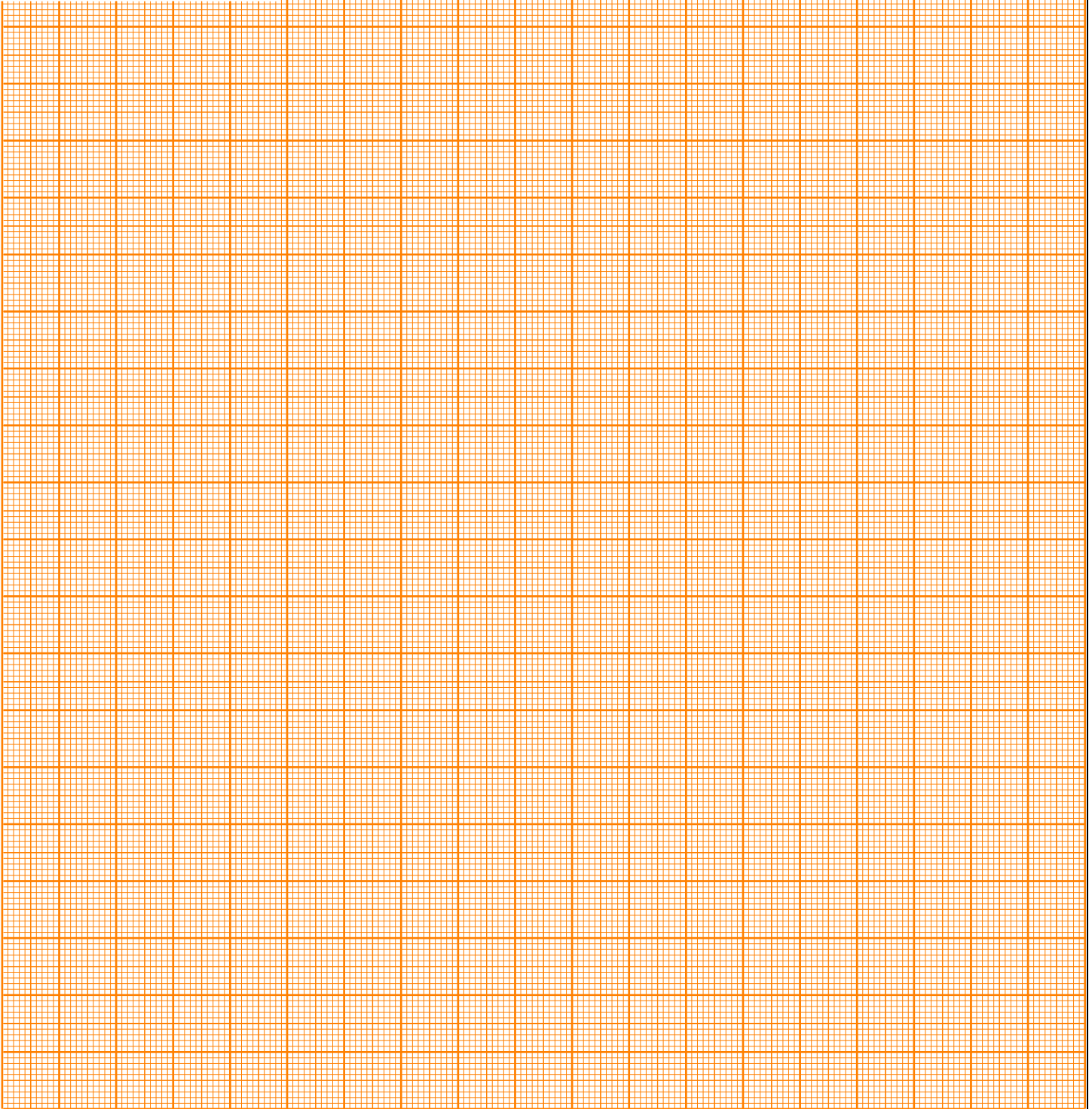


iii. (0.7 pts)  $\alpha_0 =$

iv. (1.4 pts) Use the fourth column of the table from question i.

v. (1.6 pts) Use the seventh column of the table from question i.



vi. (1 pt) Graph:  $h$  versus  $x$

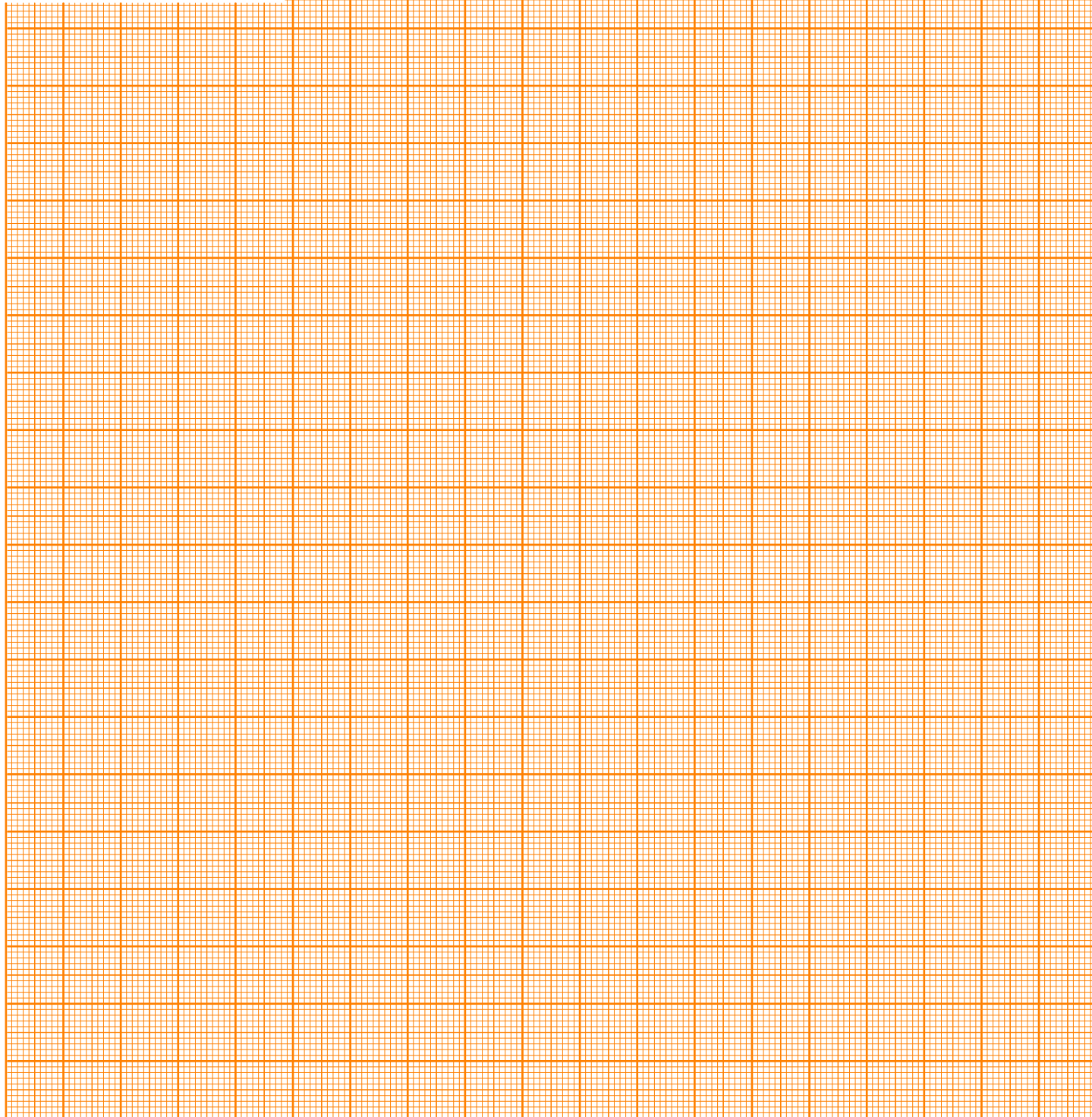

### Part C. Magnetic permeability (2 points)

Formula:  $\mu - 1 =$

Value:  $\mu - 1 =$

# ANSWER SHEET

## Problem E2



### Problem E2. Nonlinear Black Box (10 points)



#### Part A. Circuit without inductance (7 points)

i. (1 pt) Minimal and maximal current:

$$I_{\min} =$$

$$I_{\max} =$$

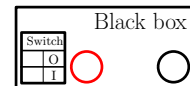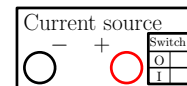Circuit diagram (mark also the positions of the switches):






ii. (1.2 pts)

$$V_0 =$$




$$C_0 =$$

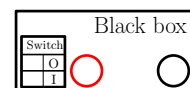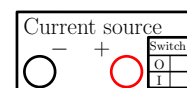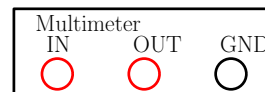Circuit diagram (mark also the positions of the switches):



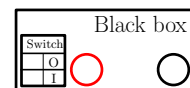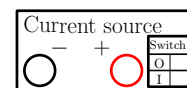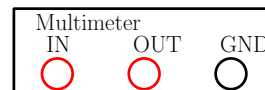iii. (2.2 pts)




Circuit diagram used for obtaining  $I(V)$  (mark also the positions of the switches):



Write the values of  $I(V)$  and any necessary intermediate results into the table on the next page. (Use as few columns as you need.) Plot the graph on page 6.

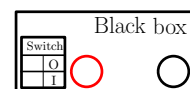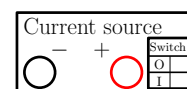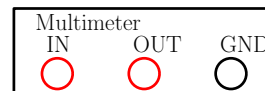iv. (2.6 pts)

Circuit diagram used for obtaining  $C(V)$  (mark also the positions of the switches):



Write the values of  $C(V)$  and any necessary intermediate results into the table on the next page. (Use as few columns as you need.) Plot the graph on page 7.


$$C_{\min} =$$

$$C_{\max} =$$






Graph:  $I$  versus  $V$

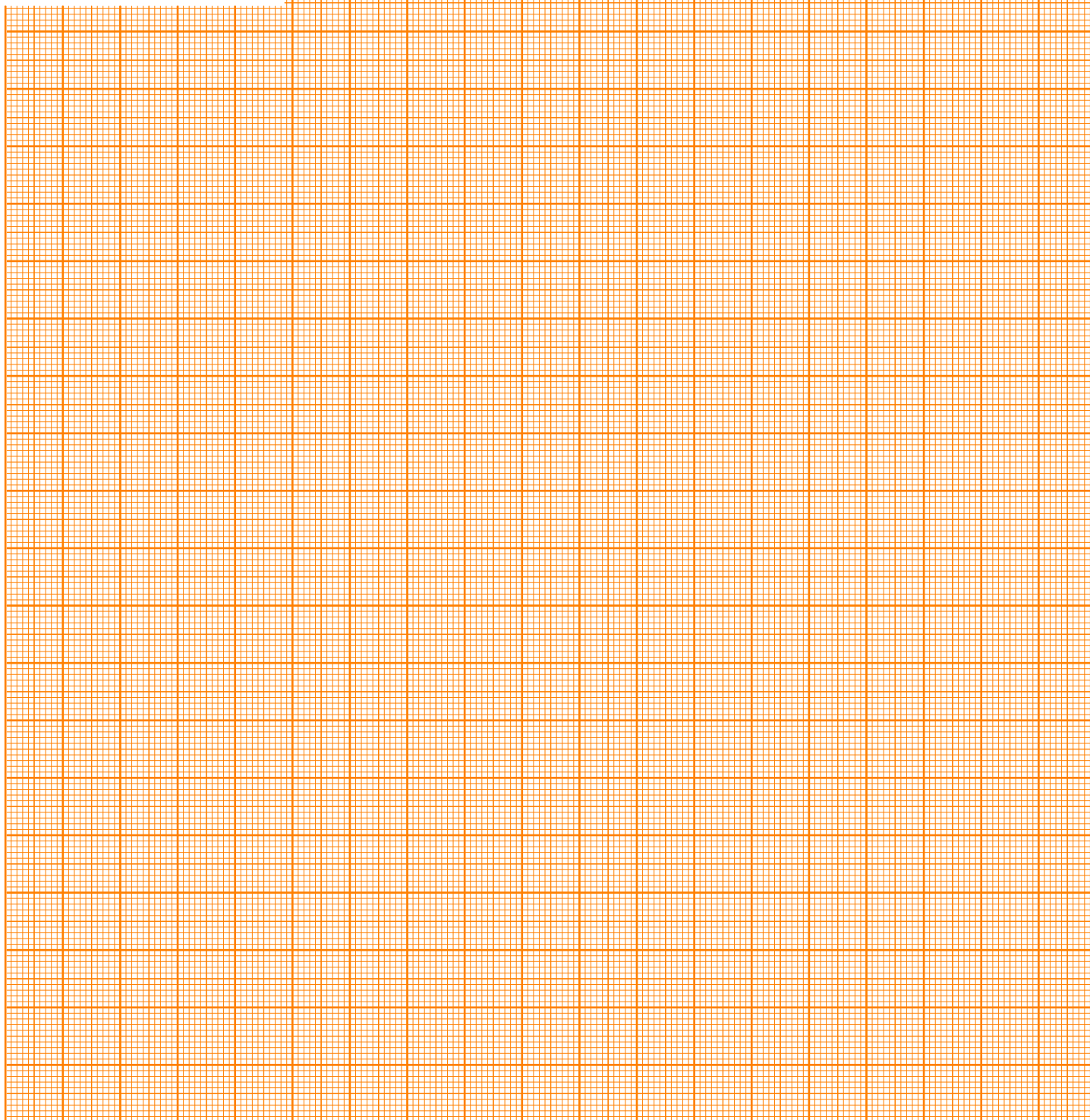



Graph:  $C$  versus  $V$

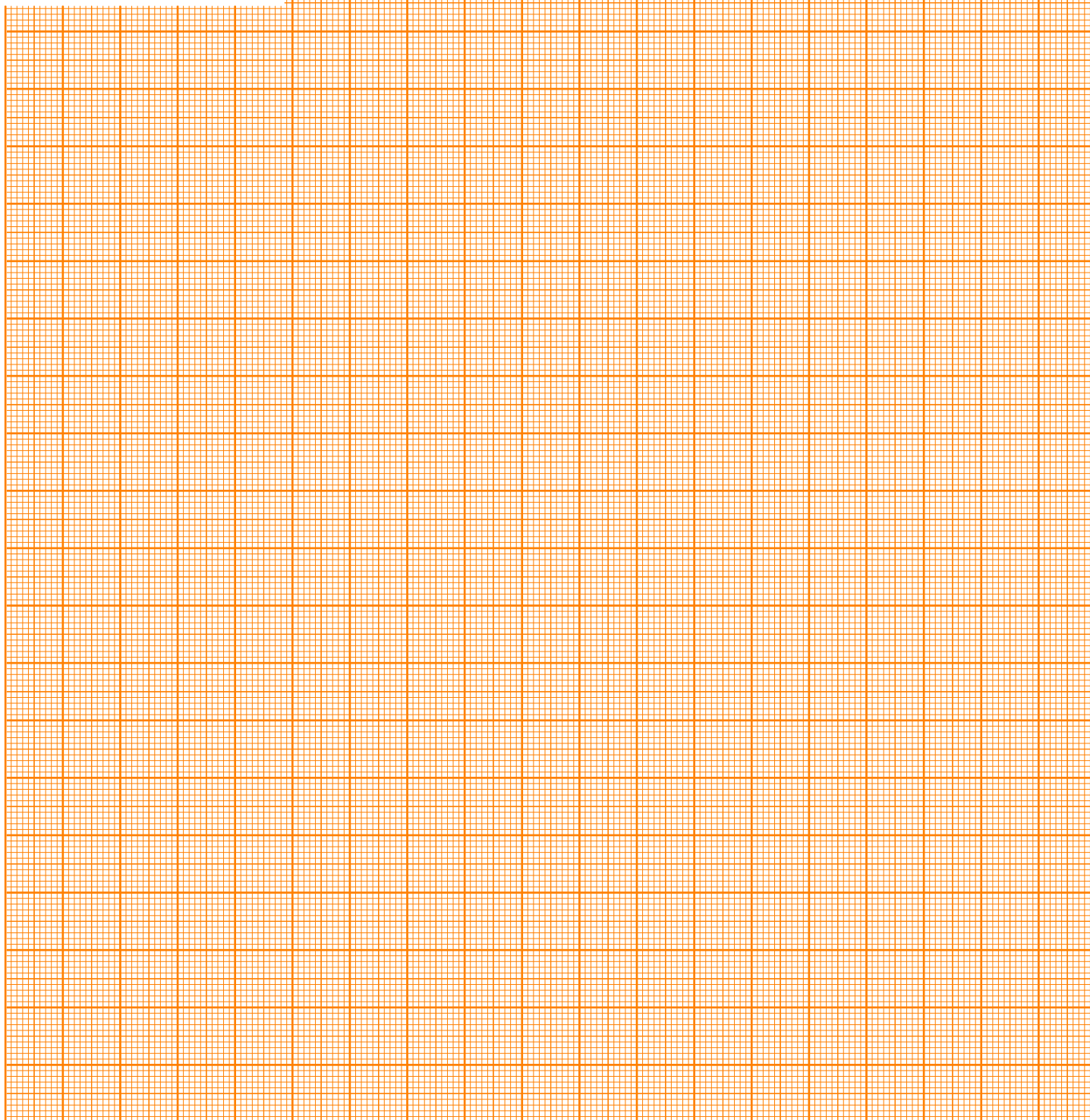








Graph:  $I$  versus  $V$

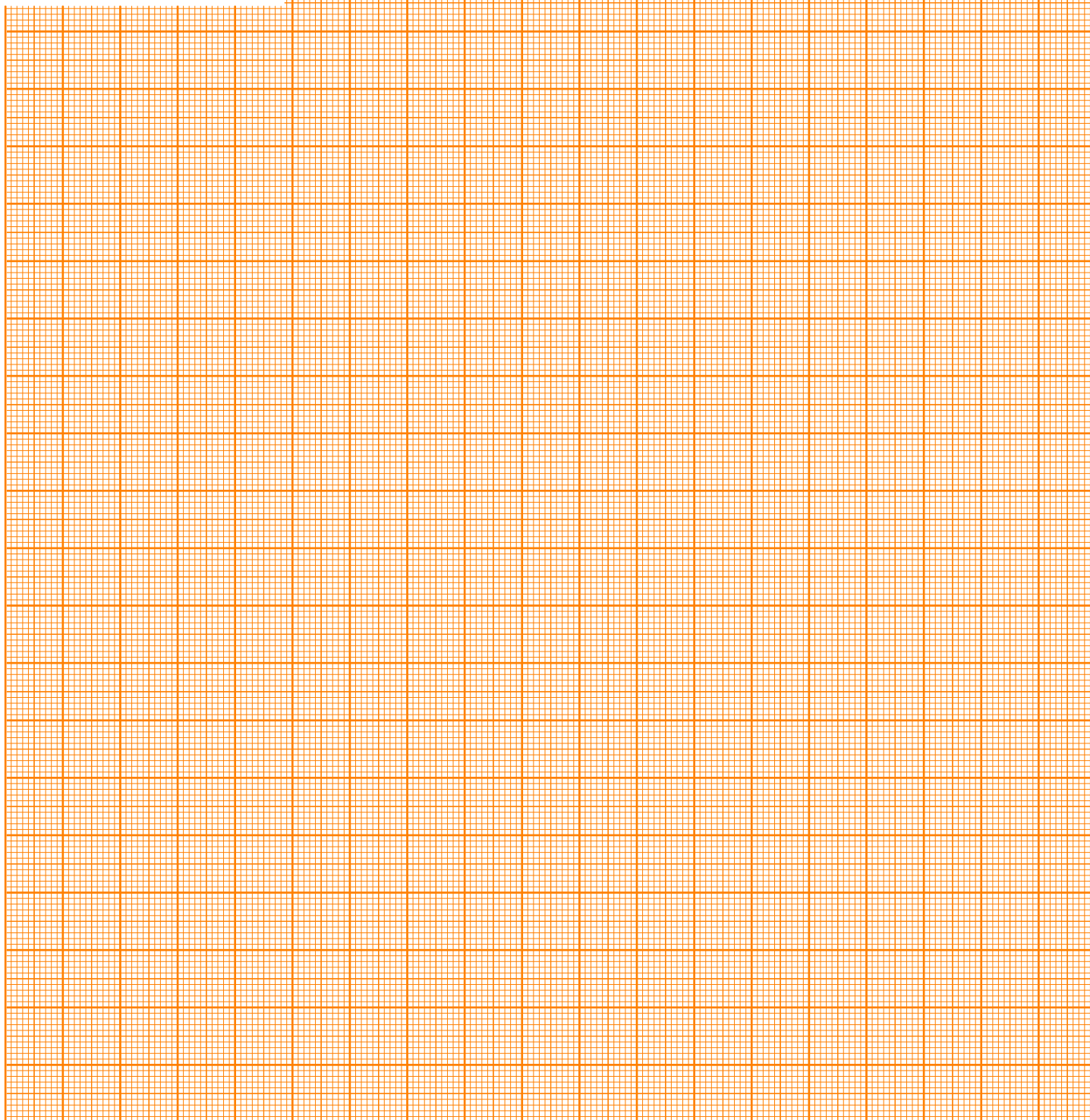

There are significant differences between the curves  
of Parts A and B when

Explanation of those differences:

Condition for $V$	
Condition for $I(V)$ from Part A	